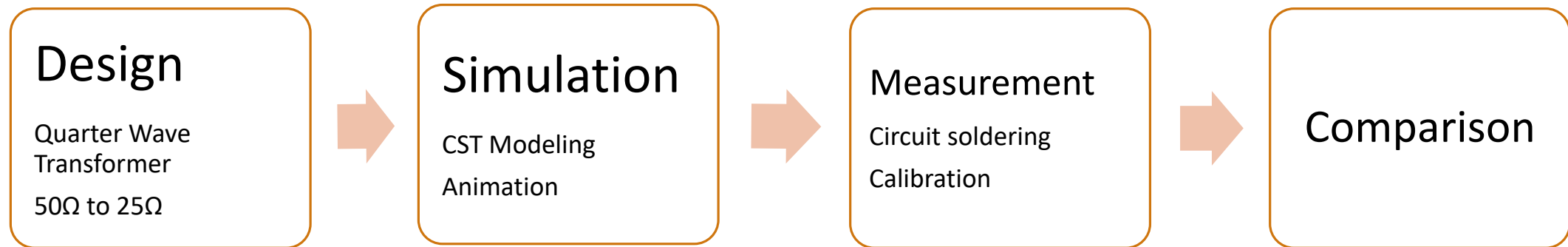


50 Ω to 25 Ω Microstrip Lines Design and Simulation

JIAWEI ZHANG, ELENA CHONG, LINGTONGYUE JIN

Overview



Quarter Wave Transformer

Impedance of Quarter-wave


$$Z_{\text{in}} = \frac{Z_c^2}{R_L}, \quad Z_c = \sqrt{Z_{\text{in}} R_L} \quad (2.62)$$

Length of Quarter-wave

$$v = \frac{1}{\sqrt{\epsilon \cdot \mu}} = \frac{3 \cdot 10^8}{\sqrt{\epsilon_r}} \frac{m}{s}$$

Effective permittivity

$$\lambda/4 = \frac{1}{4} \frac{v}{f}$$

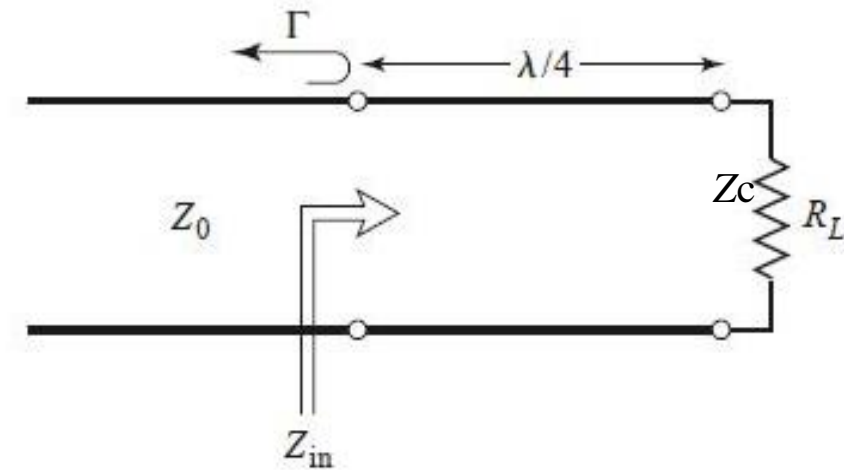

$$Z_{\text{in}} = Z_0, \quad \Gamma = 0$$

Microstrip Lines Width Calculation

Equations from Pozar

$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{(1 + 12d/W)}} \quad (3.195)$$

$$Z_0 = \frac{120 \pi}{\sqrt{\epsilon_e} \left[\frac{W}{d} + 1.393 + 0.667 \ln \left(\frac{W}{d} + 1.444 \right) \right]} \quad \text{for } W/d \geq 1 \quad (3.196)$$

Lines	Width (mm)
25Ω Line	8.375
λ/4Transformer	5.360
50Ω Line	3.277

Z₀ 25 [ohm] Synthesis >>> W 8.234375 [mm]

Z₀ 35.36 [ohm] Synthesis >>> W 5.22363281 [mm]



Z₀ 50 [ohm] Synthesis >>> W 3.17089843 [mm]

$$d = 1.160 \text{ mm}$$
$$\epsilon_r = 2.55$$

Verification from http://www1.sphere.ne.jp/i-lab/ilab/tool/ms_line_e.htm

Design Modeling & Building
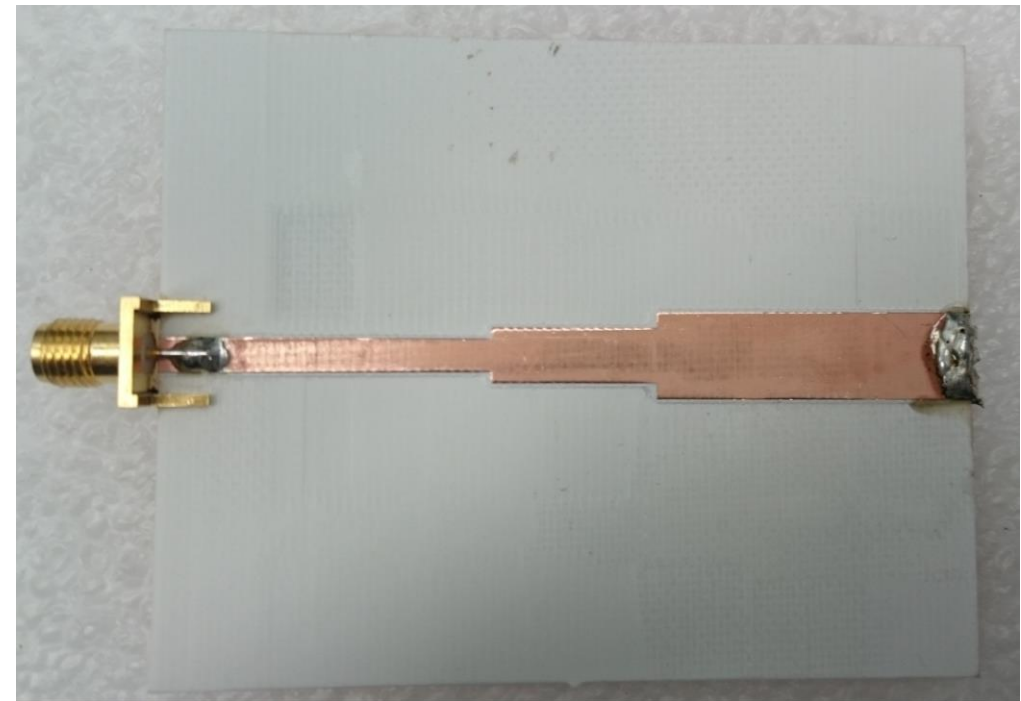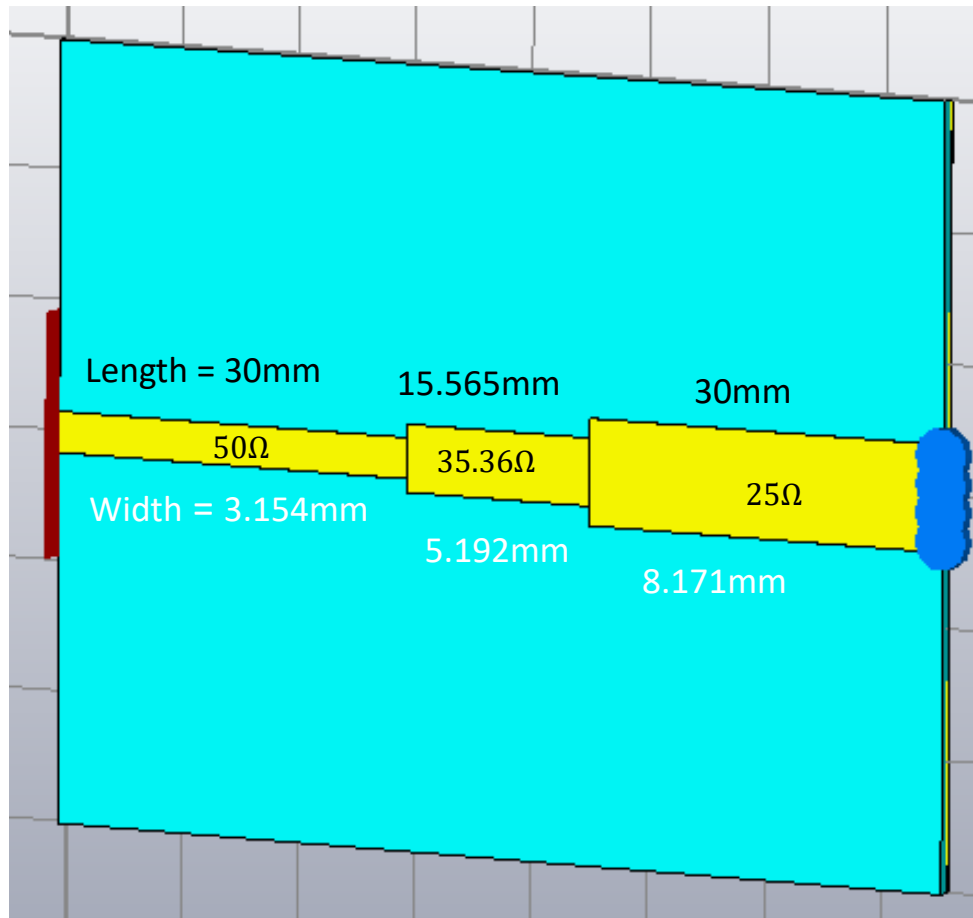
$$d = 1.160\text{mm} \quad \epsilon_r = 2.55$$



Preparing for measurement

Calibrating the Vector Network Analyzer




Short-Open-Load
Calibration

3.5mm Calibration Kit




CST Simulation

Animations in Frequency Domain

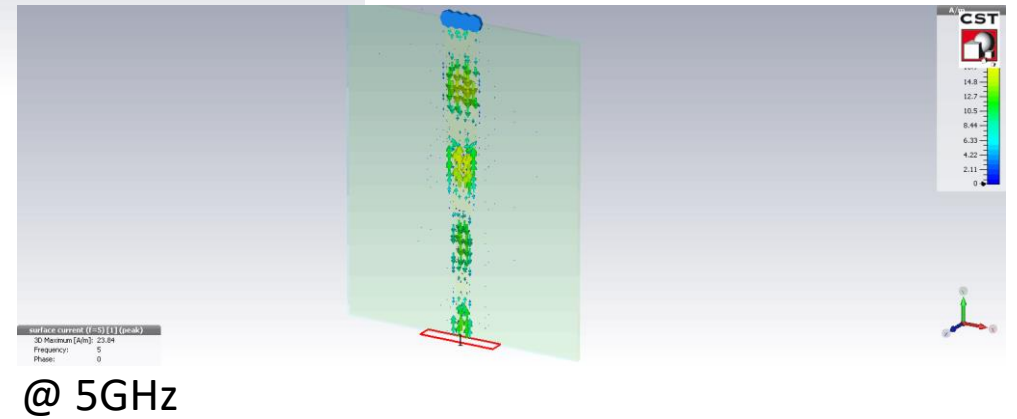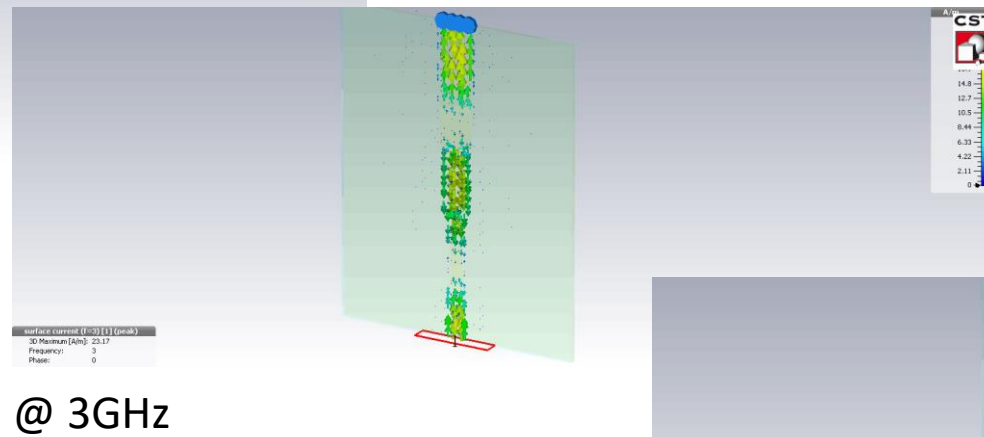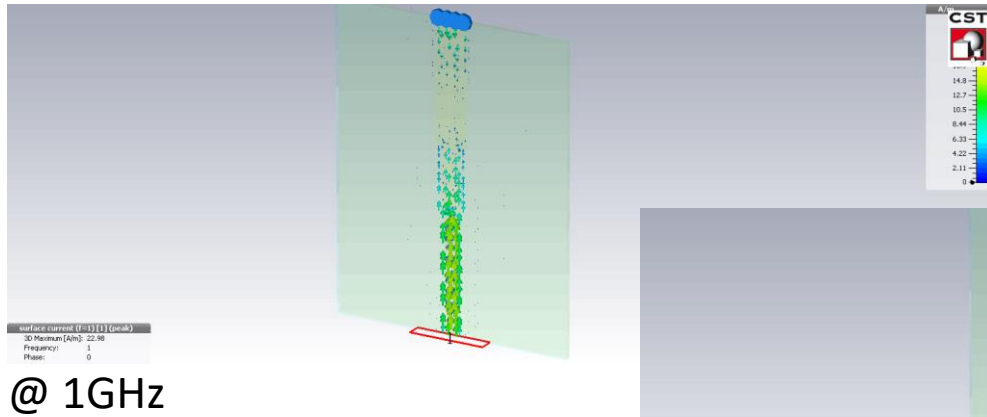

Results Comparison

Measurement & Simulation

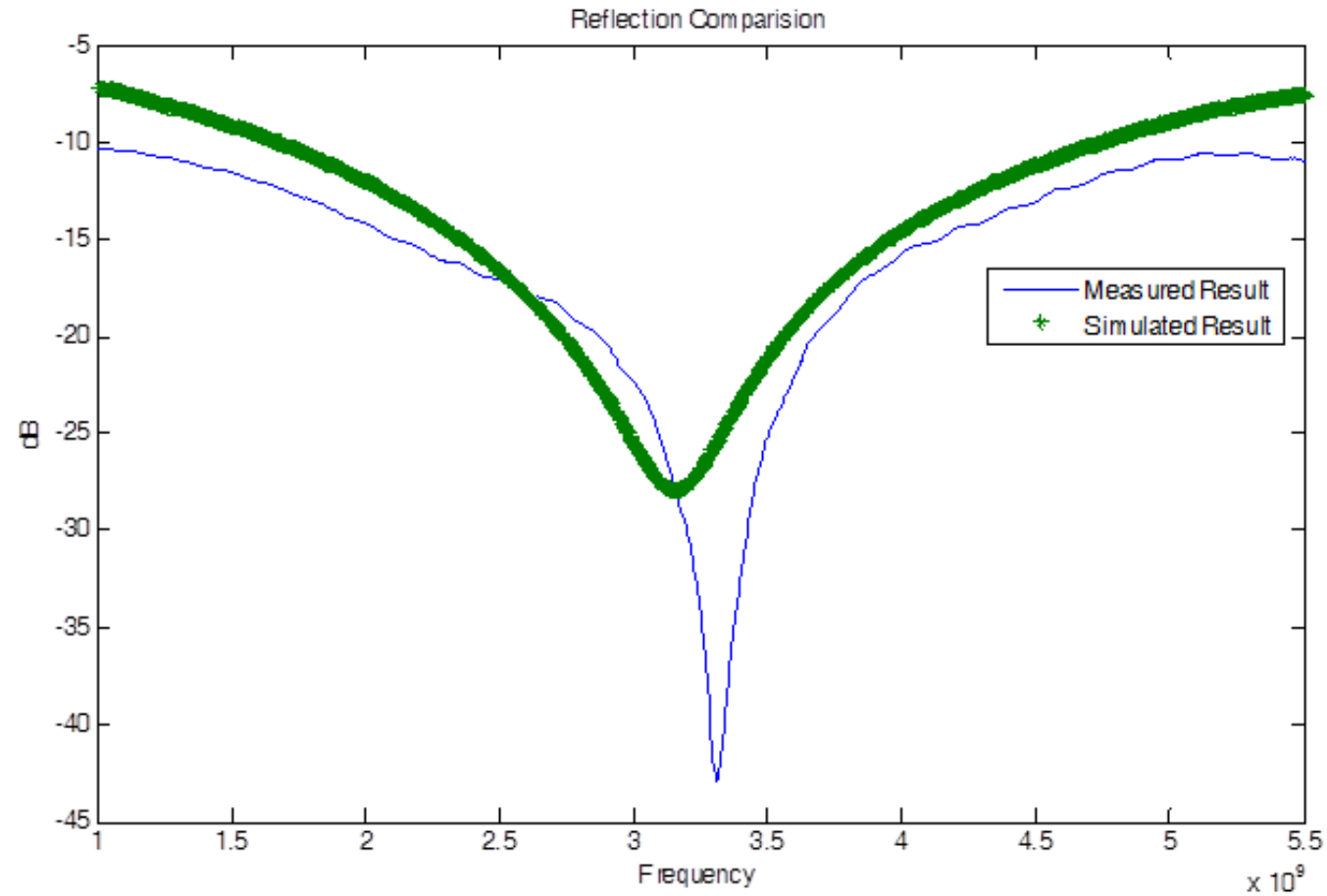

Citations

- [1] David M. Pozar, *Microwave Engineering*. Hoboken: John Wiley & Sons, Inc, 2011.
- [2] Stuart M. Wentworth, *Applied Electromagnetics: Early Transmission Lines Approach*. Hoboken: John Wiley & Sons, Inc, 2006.
- [3] “Microstrip Line Calculator.” *InfoSphere*. [Online]. Available: http://www1.sphere.ne.jp/i-lab/ilab/tool/ms_line_e.htm

Questions?